

**Cover Sheet**

**520 VLSI Design Exercise 6**

**Title: Design, layout, and simulate**

**CMOS 3-input OR circuit**

**using Cadence**

**For**

**By: Saroj Shah**

**Date: Nov 20, 2025**

**Design Exercise-6, Professor James R. Moulic**

## Introduction and Summary:


In this design exercise, using Cadence software, we are designing, laying out, and simulating a standard-cell **10-track** macro of a **0.045  $\mu\text{m}$  (45nm) CMOS 3-input OR circuit**.

## Materials:

Computer and Cadence software.

## Data:

Please refer to the screenshot provided below:

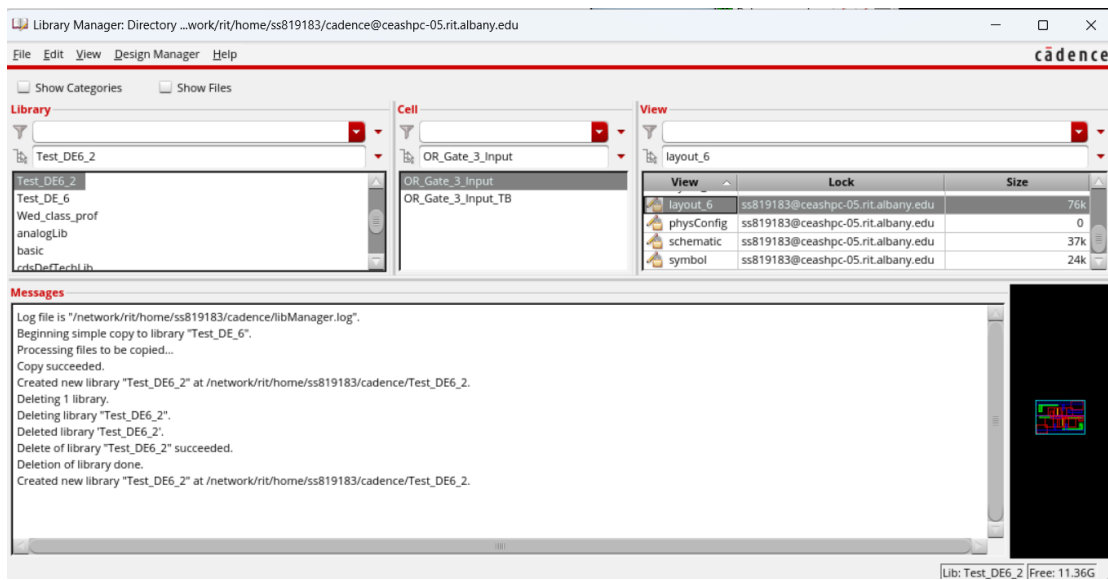

**Fig: Library manager**

## Schematic Part:


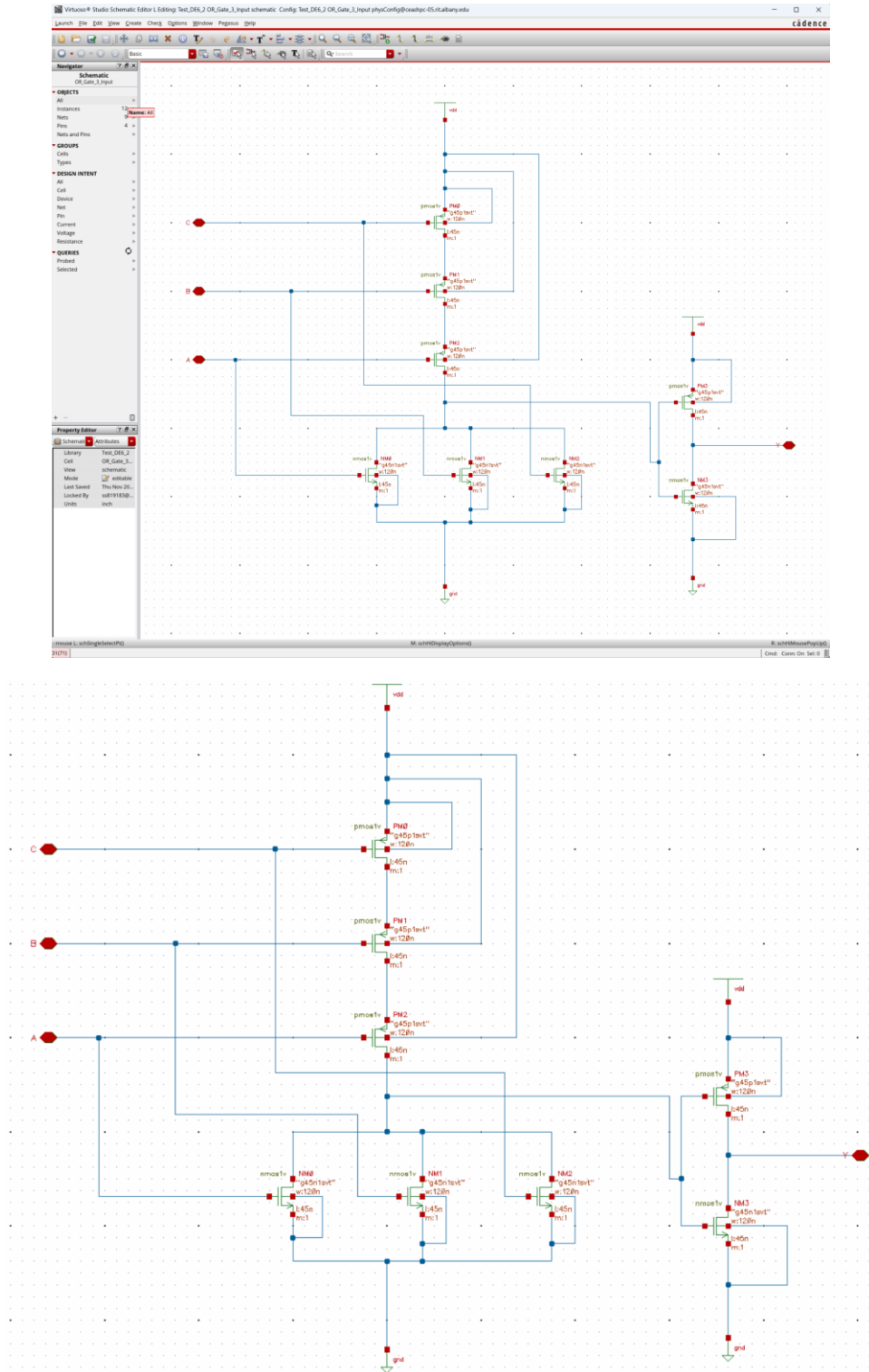



Fig: Schematic showing the OR-Gate

## Symbol creation:

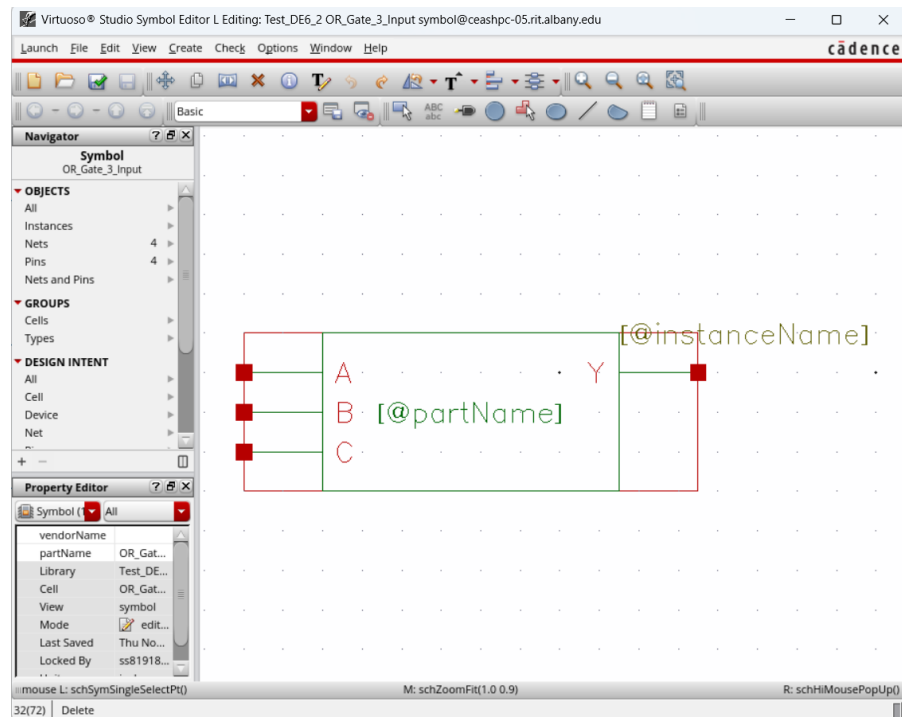

**Fig: The ‘OR’ gate schematic is symbolically represented**

## Testbench:

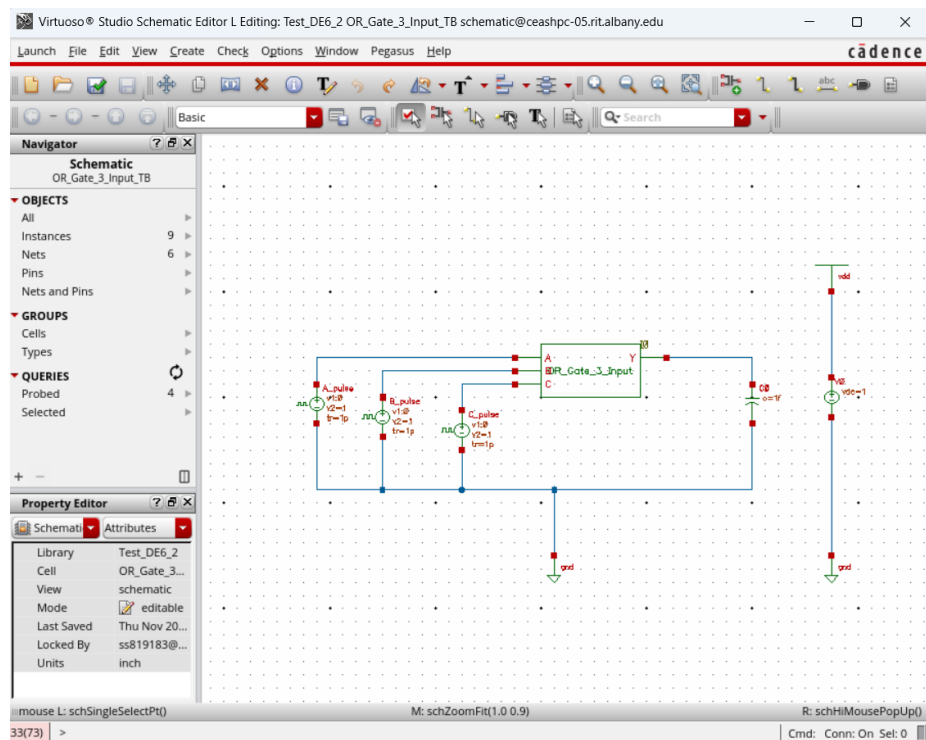

**Fig: Testbench’s Schematic**

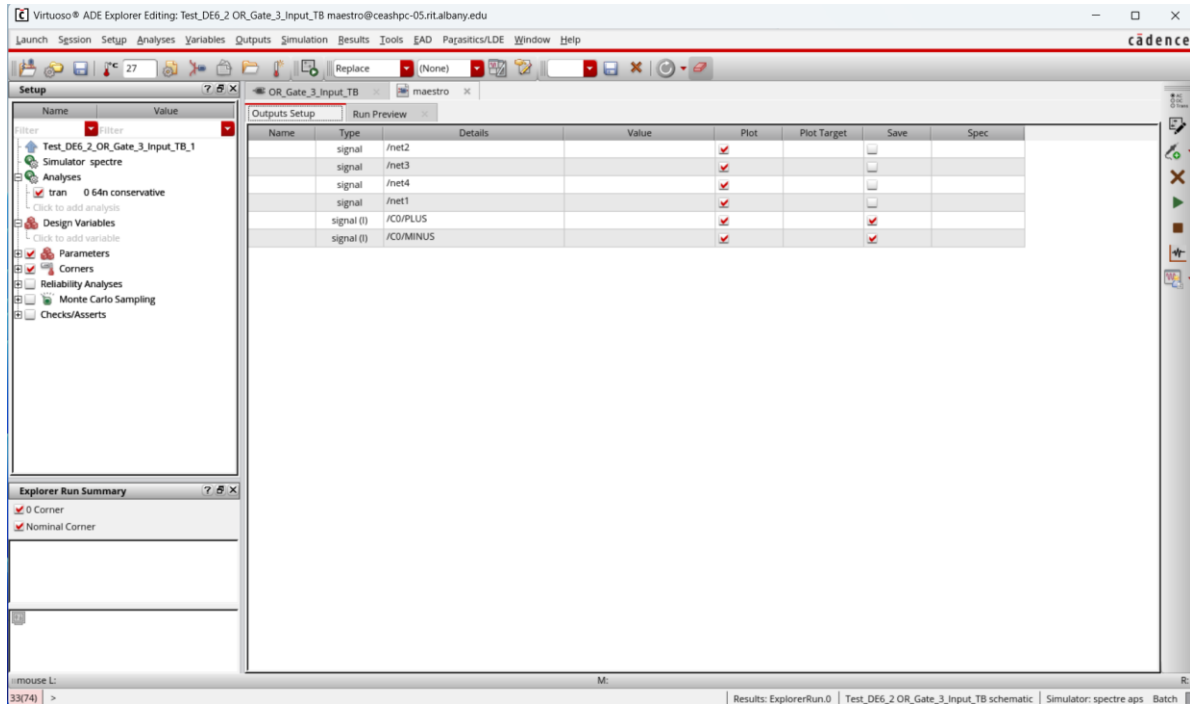


Fig: Output setup (in Maestro)



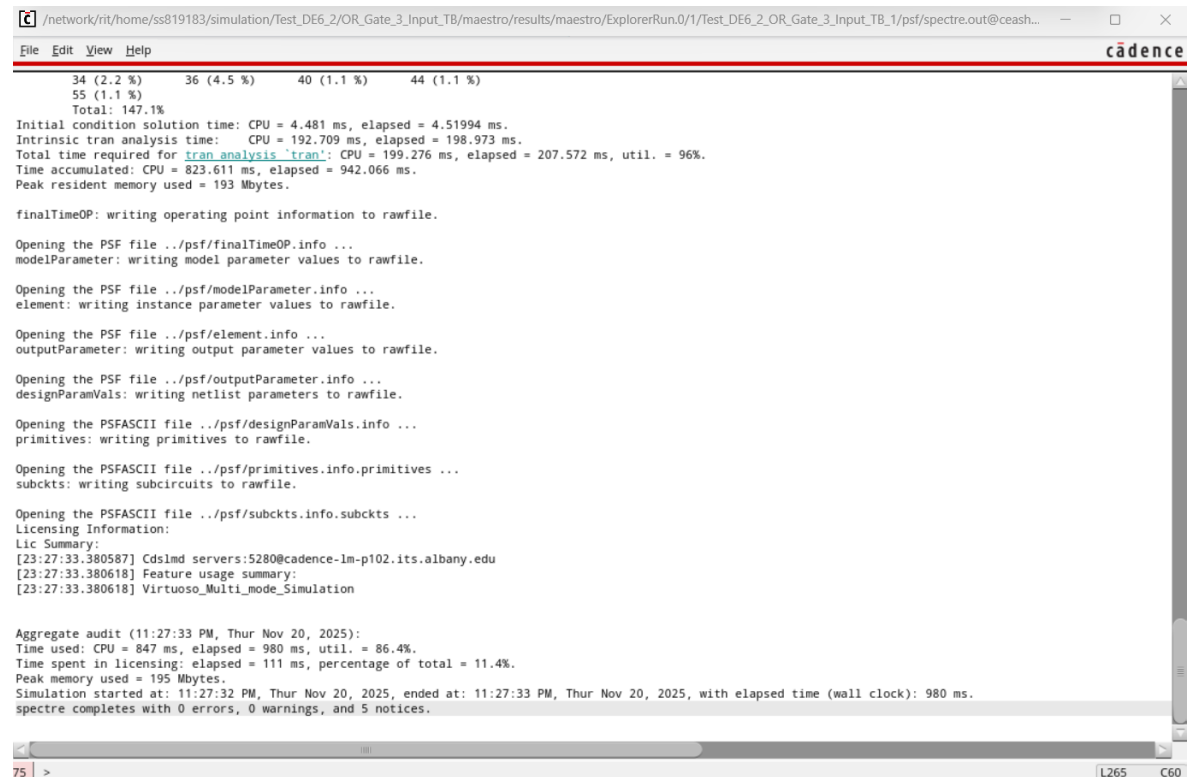


Fig: Showing portion of Netlist

## Simulation of testbench:

 

**Fig: Simulation showing Rise time: 36.59p s and source current of 28.51uA**

 

**Fig: Simulation showing Fall Time of 36.69p s and sink current of 25.40uA**

## Layout:

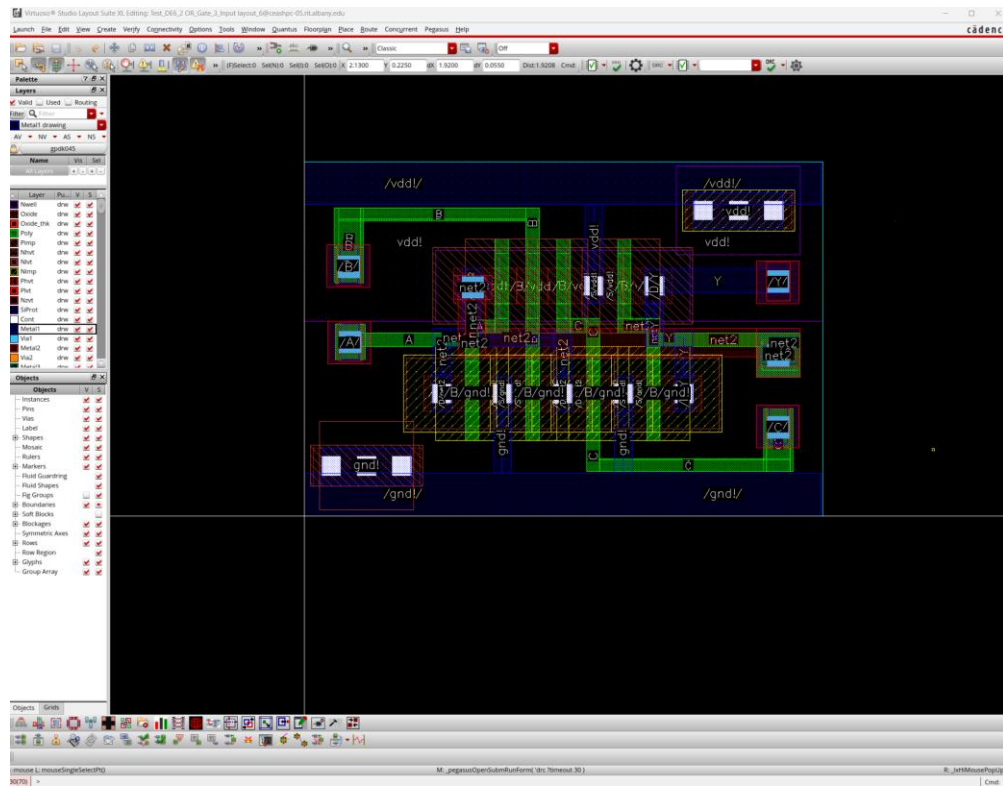


Fig: Layout


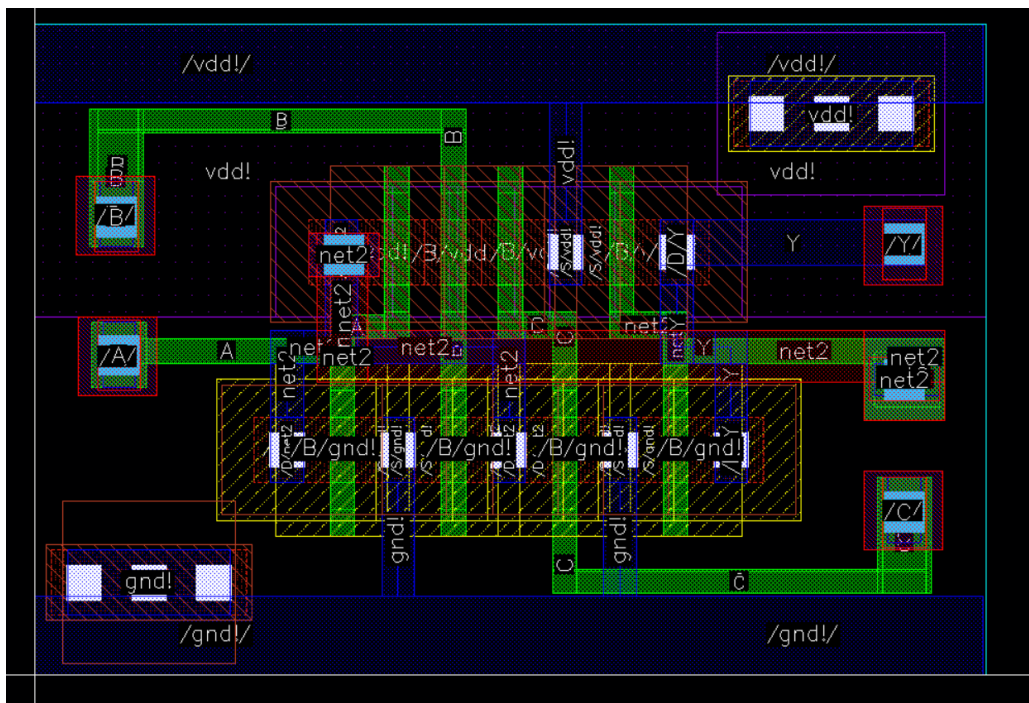
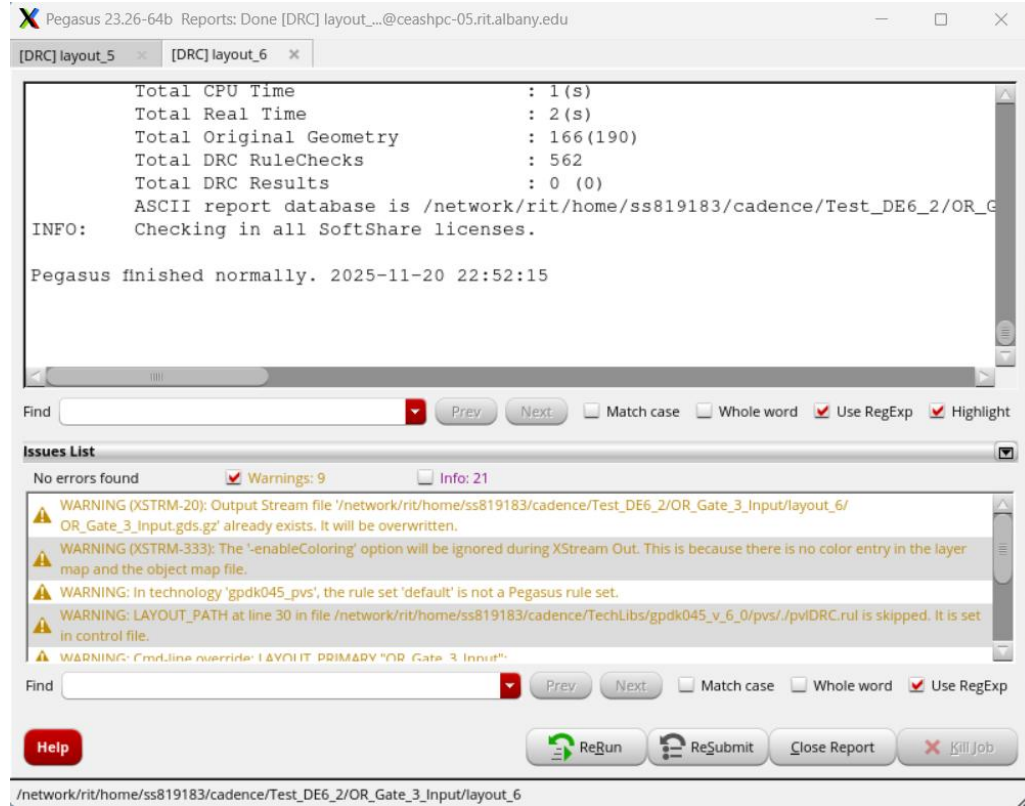


Fig: Layout in detail

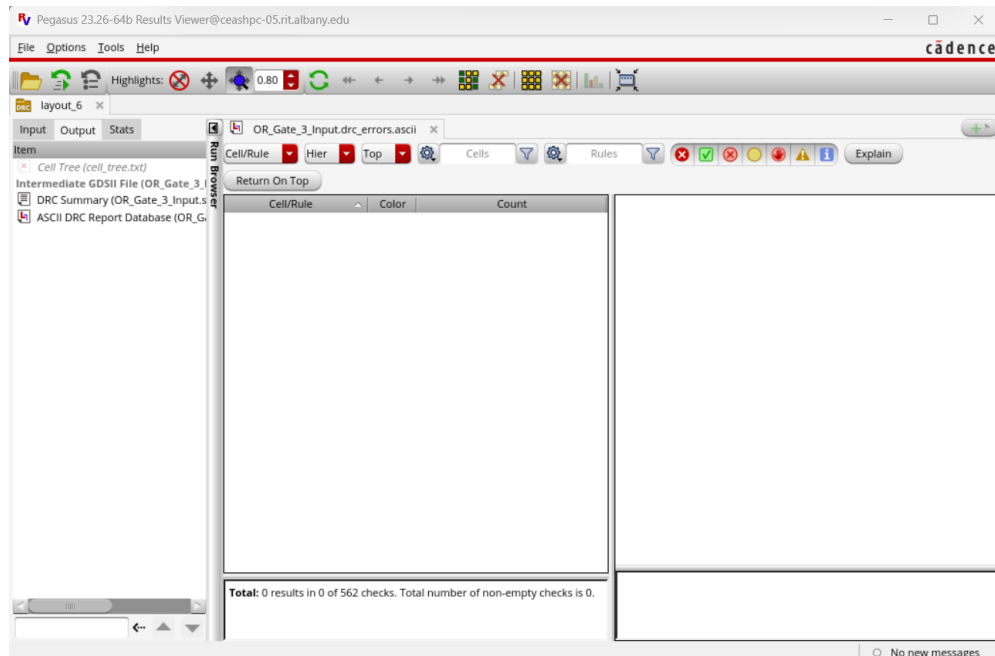**DRC Results:****Fig: DRC running****Fig: DRC Result showing absence of error**



The above DRC check shows no errors, indicating that the Layout was created successfully.

**Conclusion:**

The testbench simulation shows a rise time of 36.59 ps with a source current of 28.51  $\mu\text{A}$ , and a fall time of 36.69 ps with a sink current of 25.40  $\mu\text{A}$ . These values fall within the acceptable range specified in the problem statement. Furthermore, the absence of DRC errors confirms that the layout of the three-input OR gate has been successfully completed.

### Works Cited

Moulic, James R. Class Notes. PDF and videos.